



Série de exercícios 3

1. Calculate the capacity C of two parallel plates of area $A = 100 \text{ cm}^2$ separated by a distance $d = 1 \text{ cm} = 1 \text{ mm}$.

2. Find the area of a parallel plate capacitor with 1 cm plate separation and 1 F capacity.

3. Find the expression for the capacity of a cylindrical capacitor consisting of two conductors both of length L . One cylinder has radius r_1 and the other is a hollow cylinder (i.e. a cylindrical surface) of coaxial interior radius r_2 with $r_1 < r_2 \ll L$.

4. A capacitor with 14 cm square side plates separated by 2.0 mm is connected to a battery and charged up to 12 V.


- What is the charge on the capacitor?
- How much energy is stored in the capacitor?
- The battery is disconnected from the capacitor and the plate separation is increased to 3.5 mm. What is the capacitor energy variation?

5. Two capacitors have capacities $20 \mu\text{F}$ and $30 \mu\text{F}$. Find equivalent capacity if capacitors are connected in

- parallel.
- series.

6. A $2 \mu\text{F}$ and a $4 \mu\text{F}$ capacitor are connected in series to an 18 V battery. Find the charge and potential difference for each of the capacitors.

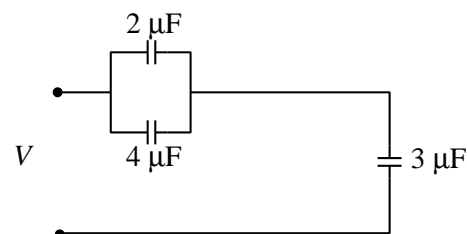7. Consider the circuit made up of the three capacitors in the figure.



- Find the equivalent capacity.
- Find the charge and voltage drop on each capacitor when the system is connected to a 6 V battery.

8. A parallel plate capacitor has 10 cm square side plates and a $d = 4 \text{ mm}$ separation. A slab with dielectric constant $\epsilon_r = 2$ has the same area as the plates.

- What is the capacity without the dielectric?
- What is the capacity if the dielectric slab fills the space between the plates?
- What is the capacity if a 3 mm thick dielectric slab is inserted into the 4 mm opening?

9. Two parallel plate capacitors, each having a capacity $C_1 = C_2 = 2 \mu\text{F}$, are connected in parallel to a 12 V battery. Find:

- The charge on each capacitor;
- The total energy stored in the capacitors.

The capacitors are then disconnected from the battery and a constant dielectric $\epsilon_r = 2.5$ is inserted between the capacitor plates C_2 . After the dielectric is inserted, find:

- the potential difference for each capacitor;
- the charge on each capacitor;
- the total energy stored in the capacitors.

Solutions:

1) $C = 8,85 \text{ pF}$; 2) $A = 0,11 \times 10^{10} \text{ m}^2$; 3) $C = \frac{2\pi\epsilon_0 L}{\ln\left(\frac{r_2}{r_1}\right)}$; 4a) $1,04 \text{ nC}$; 4b) $U = 6,24 \text{ nJ}$; 4c) $\Delta U = 4,68 \text{ nJ}$;
5a) $C_{eq} = 50 \mu\text{F}$; 5b) $C_{eq} = 12 \mu\text{F}$; 6) $Q_1 = Q_2 = 24 \mu\text{C}$; $V_1 = 12 \text{ V}$; $V_2 = 6 \text{ V}$; 7a) $C_{eq} = 2 \mu\text{F}$; 7b) $Q_1 = 4 \mu\text{C}$; $Q_2 = 8 \mu\text{C}$; $V_{12} = 2 \text{ V}$; $V_3 = 4 \text{ V}$; 8a) $C_0 = 22,1 \text{ pF}$; 8b) $C = 44,2 \text{ pF}$; 8c) $C = 35,4 \text{ pF}$; 9a) $Q = 24 \mu\text{C}$; 9b) $U = 288 \mu\text{J}$; 9c) $V = 6,86 \text{ V}$; 9d) $Q_1 = 13,7 \mu\text{C}$; $Q_2 = 34,3 \mu\text{C}$; 9e) $U = 165 \mu\text{J}$.